

**HW6:**                    **Name:** \_\_\_\_\_


**Lab Section:** \_\_\_\_\_

- 5.20 PSPICE  
MULTISIM The op amp in the circuit shown in Fig. P5.20 is ideal,
- a. Calculate  $v_o$  when  $v_g$  equals 3 V.
  - b. Specify the range of values of  $v_g$  so that the op amp operates in a linear mode.
  - c. Assume that  $v_g$  equals 5 V and that the 48 k $\Omega$  resistor is replaced with a variable resistor. What value of the variable resistor will cause the op amp to saturate?

---


**Figure P5.20**

---

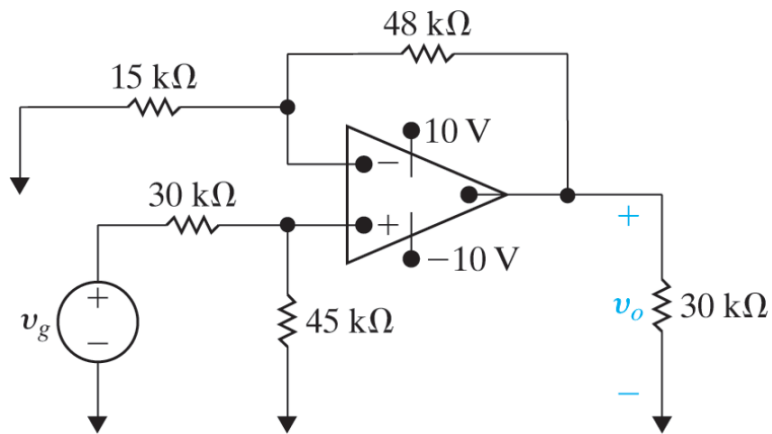

- 5.26 The resistor  $R_f$  in the circuit in Fig. P5.26 is adjusted until the ideal op amp saturates. Specify  $R_f$  in kilohms.


Figure P5.26

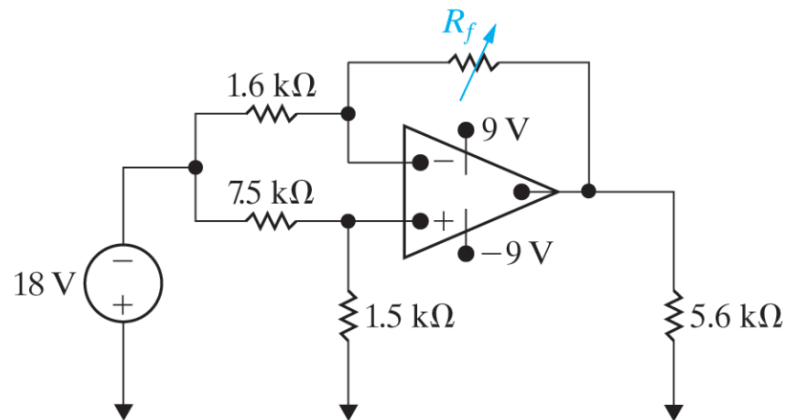

5.30 **DESIGN** PSPICE MULTISIM **PROBLEM** Select the values of  $R_b$  and  $R_f$  in the circuit in Fig. P5.30 so that

$$v_o = 8000(i_b - i_a).$$

Figure P5.30

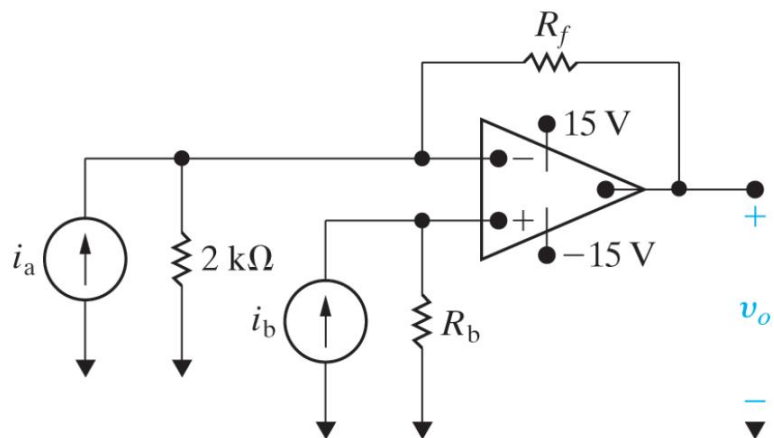


5.35 Assume that the ideal op amp in the circuit seen in Fig. P5.35 is operating in its linear region.

- Show that  $v_o = [(R_1 + R_2) / R_1]v_s$ .
- What happens if  $R_1 \rightarrow \infty$  and  $R_2 \rightarrow 0$ ?
- Explain why this circuit is referred to as a voltage follower when  $R_1 = \infty$  and  $R_2 = 0$ .

---

Figure P5.35

---

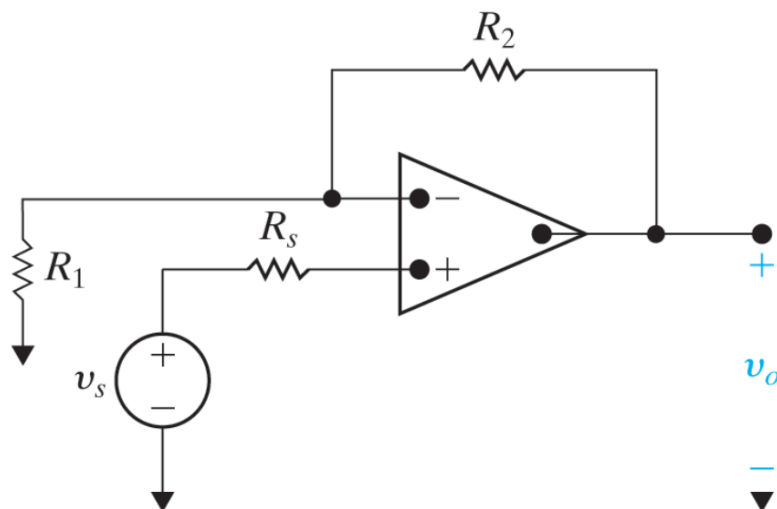


5.39 PSPICE  
MULTISIM The op amps in the circuit in Fig. P5.39 are ideal.

- a. Find  $i_a$ .
- b. Find the value of the left source voltage for which  $i_a = 0$ .

---


Figure P5.39

---

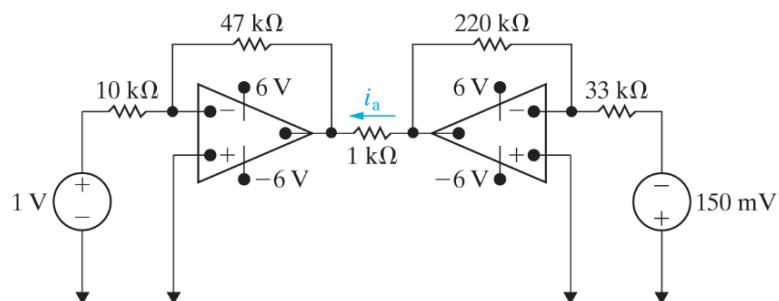

5.40 PSPICE  
MULTISIM The two op amps in the circuit in Fig. P5.40 are ideal. Calculate  $v_{o1}$  and  $v_{o2}$ .

Figure P5.40

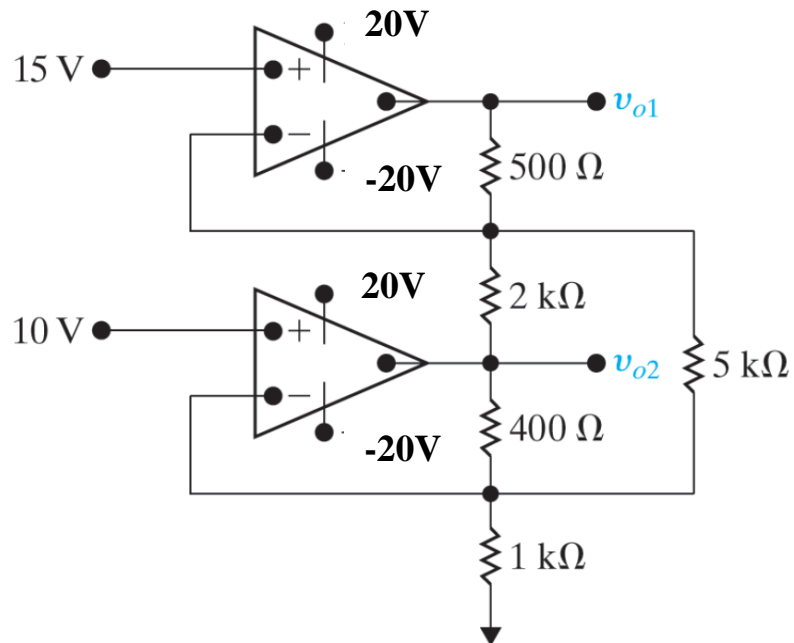

(Note: This problem is slightly modified from the P5.40 in the textbook. The 15-V supplies in the textbook is now changed to 20V)