


### The I-V Relationship for a Resistor:

From Ohm's Law we know that the voltage drop across a resistor is linearly dependent upon the current.

This is still true even if the current is a function of time.

Assume:  $i = I_m \cos(\omega t + \theta_i)$
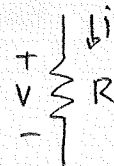
$$v = R [I_m \cos(\omega t + \theta_i)]$$



Now take the phasor transform of  $v$ .


$$\vec{V} = R I_m e^{j\theta_i} = R I_m \angle \theta_i$$

But we know that the phasor transform of  $i$  is


$$\vec{I} = I_m \angle \theta_i$$

Therefore:

$$\boxed{\vec{V} = R \vec{I}}$$

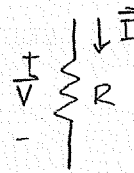

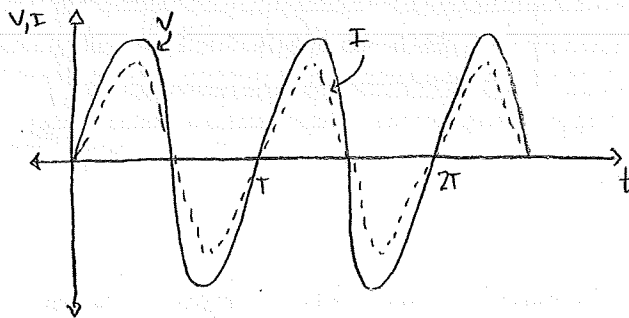This equation tells us that there is no phase shift between the voltage and current at the terminals of the resistor. They are in-phase.



### The I-V Relationship for an Inductor:


In the time domain  $v(t) = L \frac{di}{dt}$

If we assume a sinusoidal current:

$$i = I_m \cos(\omega t + \theta)$$

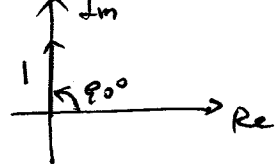(This page is from Prof. Nathan Neihart, another 201 instructor)



$$j = e^{j90^\circ} = 1 \angle 90^\circ$$


Now,  $\vec{v} = j\omega L \cdot I_m e^{j\theta} = j\omega L \cdot I_m \angle \theta^\circ$

rewrite:

$$\vec{v} = \omega L \cdot I_m e^{j(\theta+90^\circ)} = \omega L \cdot I_m \angle (\theta+90^\circ)$$

The amplitude difference is: " $\omega L$ ".


The phase difference is:  $90^\circ$  or  $\frac{\pi}{2}$ .

Therefore, there is a  $90^\circ$  phase shift between the voltage and current for an inductor!

$$i(t) = I_m \cos(\omega t + \theta)$$

$$v(t) = \omega L \cdot I_m \cdot \cos(\omega t + \theta + \underline{\underline{90^\circ}})$$

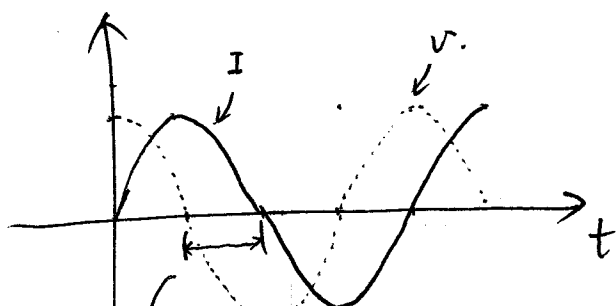The voltage leads the current, or current lags the voltage, by  $90^\circ$  or  $\frac{\pi}{2}$ .



$\frac{\pi}{2}$  in radian  
 $90^\circ$  in degree

$\frac{T}{4}$  in time


$$\left( \omega = 2\pi f = \frac{2\pi}{T} \Rightarrow \frac{T}{4} \times 2\pi = \frac{\pi}{2} \right)$$

$$\Rightarrow \frac{\pi}{2} \times T \quad (\text{from rad to } t)$$

$$\frac{90^\circ}{360^\circ} \times T \quad (\text{from degree to } t)$$

note:  $v$  reaches peaks earlier than  $i$ . "lead".

Capacitor:

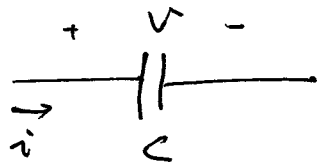

We know:  $i(t) = C \cdot \frac{dv}{dt}$ .

Now assume:  $v(t) = V_m \cos(\omega t + \theta)$ .


Using the same type of derivation that we were using for inductor, we can achieve:

$$\vec{I} = j\omega C \vec{V}$$

$$\vec{V} = \frac{1}{j\omega C} \cdot \vec{I}$$


Now, we will look at the " $\frac{1}{j}$ " term.

$$\frac{1}{j} = \frac{-j}{j \cdot (-j)} = -j$$

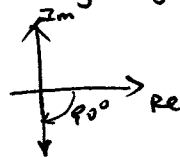$-j \Rightarrow$    $e^{-j90^\circ} = 1 \angle -90^\circ$ .

$$\vec{V} = -j \cdot \frac{1}{\omega C} \cdot \vec{I} = \frac{1}{\omega C} \angle -90^\circ \cdot \text{Im} \angle \theta^\circ = \frac{1}{\omega C} \text{Im} \angle \theta^\circ - 90^\circ$$

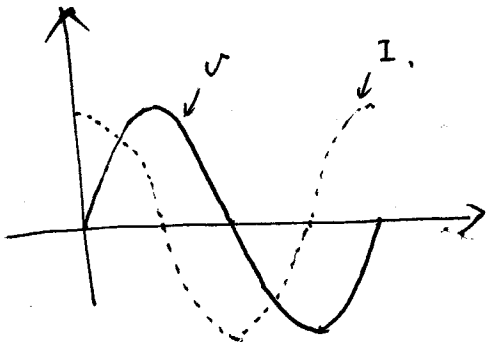Again: we see a  $90^\circ$  phase shift between the voltage and current of a capacitor.



In a cap, the current leads the voltage, or the voltage lags the current, by  $90^\circ$  ( $\frac{\pi}{2}$ ,  $\frac{I}{V}$ )

Now, we have:

$$R \Rightarrow \vec{V} = R \cdot \vec{I}$$

$$L \Rightarrow \vec{V} = j\omega L \cdot \vec{I}$$

$$C \Rightarrow \vec{V} = \frac{1}{j\omega C} \cdot \vec{I}$$

They all have a similar form:  $\vec{V} = Z \cdot \vec{I}$

Let's define:  $Z$  is the "impedance", & the impedance of an element is: the ratio of the voltage phasor

to the current phasor. In all cases,  $Z$  can be expressed

in complex number:  $Z = R + jX$ . unit is  $\Omega$  (ohm's)




$$Z = R$$

$$\rightarrow "R" = R, "X" = 0$$



$$Z = j\omega L$$

$$\rightarrow "R" = 0, "X" = \omega L$$

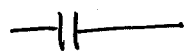

$$Z = -\frac{j}{\omega C} = \frac{1}{j\omega C}$$

$$\rightarrow "R" = 0, "X" = -\frac{1}{\omega C}$$

$$\text{in: } Z = R + jX$$



we call: resistance reactance.

Note that, passive sign convention still applies,


KVL, KCL still works.

$$\text{KVL: } \underbrace{V_1 + V_2 + \dots + V_n = 0}_{\text{original}}, \quad \underbrace{\vec{V}_1 + \vec{V}_2 + \dots + \vec{V}_n = 0}_{\text{phasor.}}$$

$$\text{KCL: } \underbrace{i_1 + i_2 + \dots + i_n = 0}_{\text{original}}, \quad \underbrace{i \vec{I}_1 + \vec{I}_2 + \dots + \vec{I}_n = 0}_{\text{phasor}}$$

Important: there is an assumption here, the frequency must be the same!
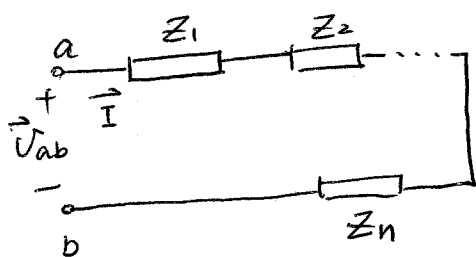
### Series and Parallel Combination of Impedances.



The rules for combining series or parallel impedance is the same as those developed for resistors.

The only difference:  $Z$  is a complex number


In series: current (either original form or phasor) must be the same.

$$\begin{aligned} \vec{V}_{ab} &= Z_1 \vec{I} + Z_2 \vec{I} + \dots + Z_n \vec{I} \\ &= \vec{I} \cdot (Z_1 + \dots + Z_n) \end{aligned}$$

$$\boxed{Z_{ab} = \sum_{i=1}^n Z_i}$$

similar to resistor.


In Parallel:

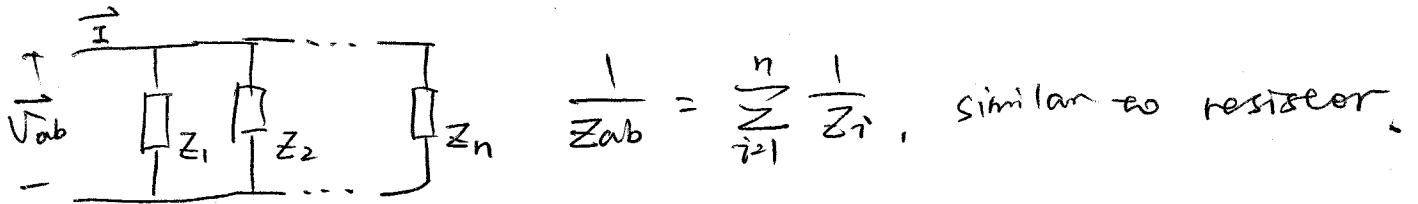

Like we define conductance:  $G = \frac{1}{R}$ .

We can define admittance:  $Y = \frac{1}{Z} = G + jB$   
Conductance      susceptance

Examples:

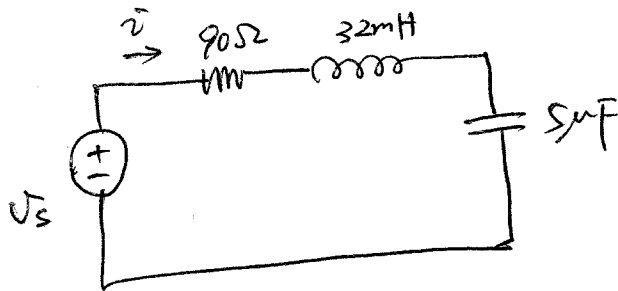

$$V_s(t) = 750 \cos(5000t + 30^\circ) \text{ V}$$

Find steady-state  $i(t)$

First of all:  $\omega = 5000 \text{ rad/s}$      $V_m = 750 \text{ V}$      $\phi = 30^\circ$

$$Z_R = 90, \quad Z_L = j\omega L = j \times 5000 \times 0.032 = j160 \Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j5000 \times 5 \times 10^{-6}} = -j40 \Omega$$


In series:  $Z = 90 + j160 - j40 = 90 + j120$ .

The phasor of  $v_s(t) \Rightarrow 750 \angle 30^\circ$ .

The phasor of  $Z \Rightarrow 90 + j120 = 150 \angle 53.13^\circ$

$$\sqrt{90^2 + 120^2}$$

$$\tan^{-1} \frac{120}{90}$$

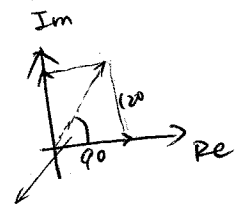

$$\vec{I} = \frac{75}{Z} = \frac{750 \angle 30^\circ}{150 \angle 53.13^\circ} = \frac{750}{150} \angle 30^\circ - 53.13^\circ$$

$$= 5 \angle -23.13^\circ$$

Multiplication

$$(A_1 \angle \phi_1^\circ) \times (A_2 \angle \phi_2^\circ) = (A_1 \times A_2) \angle (\phi_1^\circ + \phi_2^\circ)$$

Division

$$\frac{A_1 \angle \phi_1^\circ}{A_2 \angle \phi_2^\circ} = \frac{A_1}{A_2} \angle (\phi_1^\circ - \phi_2^\circ)$$

Addition:

$$A_1 \angle \phi_1^\circ + A_2 \angle \phi_2^\circ = (A_1 \cos \phi_1^\circ + A_2 \cos \phi_2^\circ) + j(A_1 \sin \phi_1^\circ + A_2 \sin \phi_2^\circ)$$

$$\Downarrow \quad \Downarrow$$

$$A_2 \cos \phi_2^\circ + j A_2 \sin \phi_2^\circ$$

$$A_1 \cos \phi_1^\circ + j A_1 \sin \phi_1^\circ$$

$$\text{Then, } \sqrt{(A_1 \cos \phi_1^\circ + A_2 \cos \phi_2^\circ)^2 + (A_1 \sin \phi_1^\circ + A_2 \sin \phi_2^\circ)^2} \angle \tan^{-1} \frac{A_1 \sin \phi_1^\circ + A_2 \sin \phi_2^\circ}{A_1 \cos \phi_1^\circ + A_2 \cos \phi_2^\circ}$$