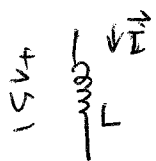


Power for Purely Inductive circuit.



For an inductor, the voltage leads the current by 90° . $\Rightarrow \theta_v = \theta_i + 90^\circ \Rightarrow \theta_v - \theta_i = 90^\circ$.

$$P_{\text{real}} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = 0 \quad \rightarrow \text{real power} = 0?$$

$$P_Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) = \frac{V_m I_m}{2} \quad \rightarrow \text{reactive power} \neq 0.$$

$$\text{So: } p(t) = P_{\text{real}} + P_{\text{real}} \cos(2\omega t) - Q \sin(2\omega t)$$


$$= -Q \sin(2\omega t) = -\frac{V_m I_m}{2} \sin 2\omega t,$$

Observation: - In a pure inductive circuit, $\int_{t_0}^{t_0+T} p(t) dt = 0$, the energy consumption is "0".

- No electric energy is transformed to Non-electric energy.

- Power is exchanged, but not consumed between the inductive circuit and the source driving the circuit at a rate of 2ω .

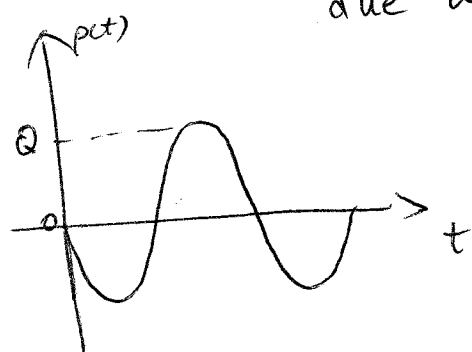
- In reality, since there are series resistance in ~~inductor~~, such as wires, so because of the AC current, there ~~may~~ be energy consumed due to the resistance in the circuit.



- when $p(t)$ is positive, energy is being stored in the inductor (magnetic field)

- when $p(t)$ is negative, energy is being extracted from the inductor (magnetic field) and goes back to the source.

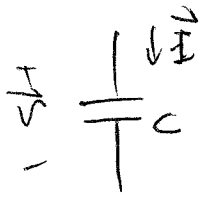Power for the Purely Capacitive circuits.



In a capacitor, the current leads the voltage by 90° , $\theta_i = \theta_v + 90^\circ \Rightarrow \theta_v - \theta_i = -90^\circ$.


Similarly: $P_{real} = \frac{V_m I_m}{2} \cos(-90^\circ) = 0$.

$$Q = \frac{V_m I_m}{2} \sin(-90^\circ) = -\frac{V_m I_m}{2}$$

$$\Rightarrow p(t) = -Q \sin(2\omega t) = \frac{V_m I_m}{2} \sin 2\omega t.$$

$\int_{t_0}^{t_0+T} p(t) dt = 0$. no energy is consumed by capacitive circuit.

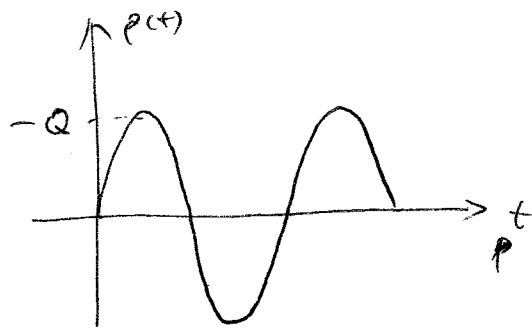Like inductors, Energy is exchanged between the source driving the capacitive circuit, & the electric field of the capacitive circuit.



As for $p(t)$, $P_{real} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$, $Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$

The angle " $\theta_v - \theta_i$ " is referred to as the power factor angle.

$$\cos(\theta_v - \theta_i) \leftarrow \text{power factor (pf)}$$

$$\sin(\theta_v - \theta_i) \leftarrow \text{reactive factor (rf)},$$

usually, an electronic product will show their power factor,

but knowing the power factor does not tell you the value of

b. the power factor angle, because,


$$\cos(\theta_v - \theta_i) = \cos(\theta_i - \theta_v)$$

To completely describe this angle, engineers use the following describing terms:

Lagging power factor : current lags the voltage.
 \Rightarrow inductive load.

Leading power factor : current leads the voltage.
 \Rightarrow Capacitive load.

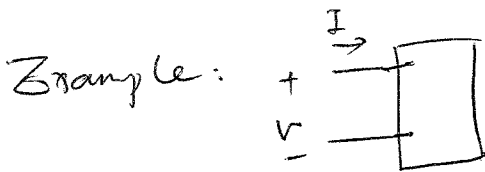The power factor or reactive factor are convenient ways to describe electrical loads.



Assume: $v(t) = 100 \cos(\omega t + 15^\circ) \text{ V}$
 $i(t) = 4 \sin(\omega t - 15^\circ) \text{ A}$.

Find the average power & the reactive power.

First, the current is expressed in "sin", let's convert it to "cos" : $\sin\theta = \cos(\theta - 90^\circ)$

$$i(t) = 4 \sin(\omega t - 15^\circ) = 4 \cos(\omega t - 105^\circ)$$

Now, find P_{real} and Q .

$$P_{\text{real}} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = \frac{100 \times 4}{2} \times \cos[15^\circ - (-105^\circ)]$$

$$= 200 \times \cos 120^\circ = -100 \text{ W}$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) = 200 \times \sin 120^\circ = 173 \text{ Var}$$

From passive sign convention, $P_{\text{real}} = -100 \text{ W}$,
 \uparrow
 negative.

The device is developing power.
 \uparrow
 average

rms power.

We have introduced this previously:


for $v(t) = V_m \cos(\omega t + \theta_0)$, if a load R is attached:




$$\begin{aligned}
 P &= \frac{1}{T} \int_{t_0}^{t_0+T} p(t) dt = \frac{1}{T} \int_{t_0}^{t_0+T} \frac{V_m^2 \cos^2(\omega t + \theta_0)}{R} dt \\
 &= \frac{1}{R} \times \underbrace{\frac{1}{T} \int_{t_0}^{t_0+T} v(t) dt}_{V_{rms}} \\
 &= \frac{V_{rms}^2}{R}
 \end{aligned}$$

or: $p = I_{rms}^2 R$.

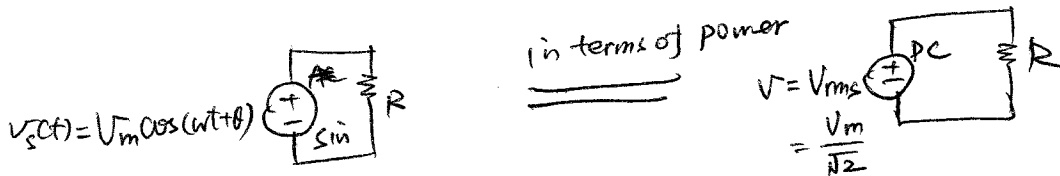The power generated by $v(t) = V_m \cos(\omega t + \theta)$ delivered to R , is the same as a DC source with a value V_{rms} .



Example:

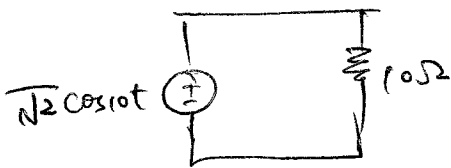

the $v(t) = \sqrt{2} \cos 10t$

$$V_{rms} = \frac{\sqrt{2}}{\sqrt{2}} = 1V$$

$$P = \frac{V_{rms}^2}{R} = \frac{1^2}{10} = 0.1 W$$

Energy delivered to the load in 1s: $\int_0^1 0.1 dt = 100mJ$

Same as $P = \frac{V^2}{R} = 0.1W$, energy in 1s: $\int_0^1 0.1 dt = 100mJ$

The book sometimes refers to the RMS value as the effective value.

$$P_{\text{real}} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

can be rewritten as: $P_{\text{real}} = \frac{V_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i)$

$$= V_{\text{eff}} \times I_{\text{eff}} \cos(\theta_v - \theta_i)$$

$$Q = V_{\text{eff}} I_{\text{eff}} \sin(\theta_v - \theta_i)$$

Complex Power

The complex sum of average power and reactive power.


$$S = P + jQ$$

(here P_{real} we write it as P)

unit?

Watt Var

VA !! Volt-amp. (common for P & Q)

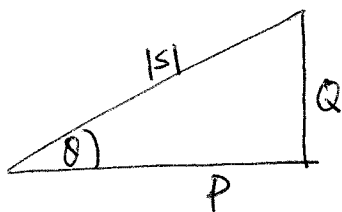

(P_{real})

power triangle

$$|S| = \sqrt{P^2 + Q^2}$$

$$\theta = \theta_v - \theta_i, \quad \tan \theta = \frac{Q}{P}$$

Remember: $Q = \frac{I_m V_m}{2} \sin(\theta_v - \theta_i)$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$\frac{Q}{P} = \tan(\theta_v - \theta_i)$$

the term $|S|$ is referred to as apparent power.

Usually, the apparent power is more important than the average power.

- The ~~measured~~ average or real power is a measure of how much electric energy to non-electric energy.
- The reactive power is a measure of how much energy goes into charging up all of the reactive elements in a circuit.
- The apparent power is a measure of how many Volt-amp is required from the supply in order to supply the average power.

This is important because if :

design A requires 100 VA to generate an average power of 10W.

design B requires 20 VA to generate the same average power of 10W.

clearly, design B is a better design, (efficient)

the power triangle is a convenient tool to visualize how the average power, reactive power, & the apparent power all relate.

For maximum efficiency we want the reactive power ~~to~~ to be as small as possible, (power factor to be as close ~~as~~ to 1 as possible)

f. If $\theta_v = \theta_i$, $\cos(\theta_v - \theta_i) = 1$, $pf = 1$, apparent power = average power, reactive power = 0.