
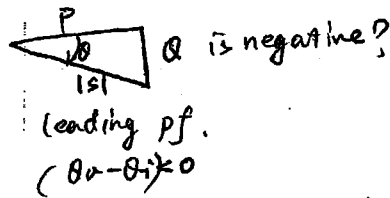


Complex Power Cont.

$$S = P + jQ$$

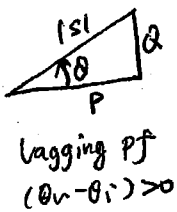\uparrow average/real power
 \uparrow reactive power.



$$S = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + j \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$

$$= \frac{V_m I_m}{2} \left[\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i) \right]$$

$$= \frac{V_m I_m}{2} e^{j(\theta_v - \theta_i)} = \frac{1}{2} V_m I_m \angle(\theta_v - \theta_i)$$

Using the rms or effective value, $V_{eff} = \frac{V_m}{\sqrt{2}}$, $I_{eff} = \frac{I_m}{\sqrt{2}}$

$$S = V_{eff} I_{eff} \angle(\theta_v - \theta_i)$$

We now have "S" in terms of phasors

$$S = V_{eff} I_{eff} e^{j\theta_v} e^{-j\theta_i}$$

$$= \frac{V_{eff} e^{j\theta_v}}{\downarrow} \cdot \frac{I_{eff} e^{-j\theta_i}}{\downarrow}$$

?? consider: $I_{eff} e^{-j\theta_i} = I_{eff} [\cos \theta_i - j \sin \theta_i]$

while: $\overline{I_{eff}} = I_{eff} e^{j\theta_i} = I_{eff} [\cos \theta_i + j \sin \theta_i]$

So, $I_{eff} e^{-j\theta_i} = \overline{I_{eff}}^*$, The complex conjugate of $\overline{I_{eff}}$.

$$\Rightarrow S = \overline{V_{eff}} \cdot \overline{I_{eff}}^* \quad (\text{expressed in terms of rms, eff})$$

Or, if using amplitude: $\vec{V}_{eff} = \frac{\vec{V}}{\sqrt{2}}$, $\vec{I}_{eff} = \frac{\vec{I}}{\sqrt{2}}$

$S = \frac{1}{2} \vec{V} \cdot \vec{I}^*$, still, \vec{I}^* is the complex conjugate of \vec{I} .

Also, for complex power:

$$S = |\vec{I}_{eff}|^2 \cdot Z$$

$$S = \frac{|\vec{V}_{eff}|^2}{Z^*}$$


where $Z = R + jX$

So, it leads to: $P = |\vec{I}_{eff}|^2 \cdot R = \frac{1}{2} I_m^2 R$, $Q = |\vec{I}_{eff}|^2 \cdot X = \frac{1}{2} I_m^2 X$

While $P = \frac{|\vec{V}_{eff}|^2}{R} = \frac{V_m^2}{2R}$
is only true with
a pure resistive
component

$Q = \frac{|\vec{V}_{eff}|^2}{X} = \frac{V_m^2}{2X}$
is only true with
a pure reactive
component.

Example:

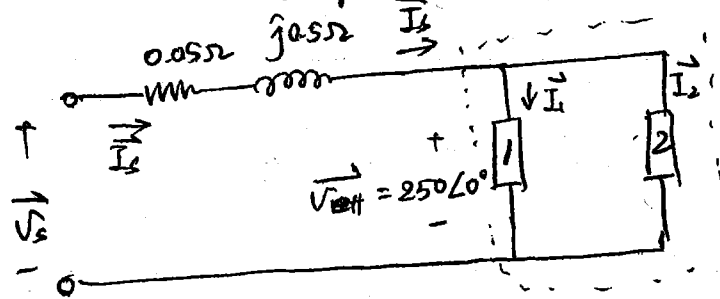

Load 1 absorbs an average power of 8KW, at a leading power factor of 0.8; Load 2 absorbs 20KVA at a lagging power factor of 0.6.

Q. Determine the power factor of the 2 loads in Parallel, here, all currents & voltages are effective "rms" values.

From the schematic: $\vec{I}_s = \vec{I}_1 + \vec{I}_2$.

The complex power of the parallel circuit:

b:

$$S = \vec{V}_{eff} \cdot \vec{I}_s^* = 250 \angle 0^\circ \times (\vec{I}_1 + \vec{I}_2)^*$$

$$= 250 \angle 0^\circ \times \vec{I}_1^* + 250 \angle 0^\circ \times \vec{I}_2^*$$

$$S = \underline{S_1 + S_2}$$

It's the sum of complex power of the two loads.

So, let's look at load 1.


We know $P_1 = 8 \text{ kW}$, a leading power factor of 0.8

$$\theta_i - \theta_v > 0, \text{ so } \theta = \theta_v - \theta_i < 0$$

$$\sin \theta < 0.$$

$$Q = - \sin \theta < 0.$$

draw the power triangle:

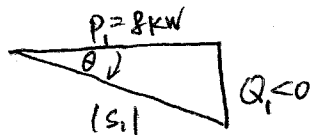


$$\cos \theta = 0.8, \text{ so: } |S_1| = \frac{8 \text{ K}}{0.8} = 10 \text{ K VA.}$$

$$Q_1 = -6 \text{ K VAR.}$$

$$\boxed{S_1 = 8 \text{ K} - j6 \text{ K}}$$

Then let's look at load 2.

$|S_2| = 20 \text{ K VA}$, lagging power factor of 0.6
apparent power.

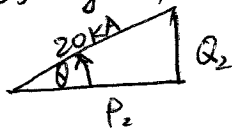


$$\cos \theta = 0.6 \Rightarrow P_2 = 0.6 \times 20 \text{ K} = 12 \text{ kW.}$$

$$Q_2 = \sqrt{20 \text{ K}^2 - 12 \text{ K}^2} = 16 \text{ K VAR}$$

$$\boxed{S_2 = 12 \text{ K} + j16 \text{ K}}$$

$$S = S_1 + S_2 = 20 \text{ K} + j10 \text{ K.}$$

power factor?

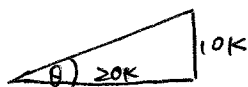

$$\cos \theta = \frac{20 \text{ K}}{\sqrt{(20 \text{ K})^2 + (10 \text{ K})^2}} = 0.894 \text{ (pf)}$$

C.