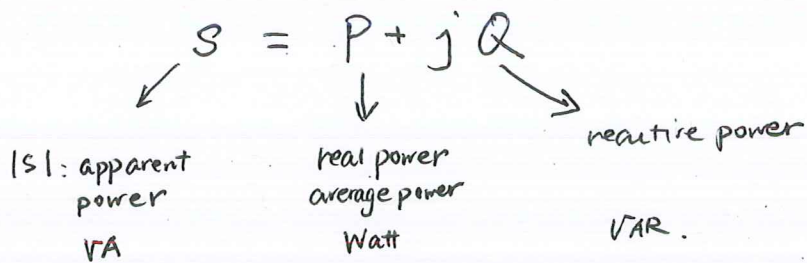



previously, we have introduced complex power:



$P$ : the measure of how much electric <sup>power</sup> energy is converted to non-electric ~~energy~~ power. (heat, motion, ...)

$Q$ : the measure of how much power goes to charge up all the reactive elements in a circuit. (such the magnetic field in a motor)

$|S|$ : the measure of how much Volt-amp is required to supply in order to supply the  $P$  (make the work done)

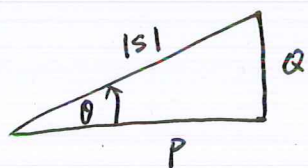

$Q$  is positive  
current lags voltage.

$$\theta_i - \theta_v > 0$$

(lagging (inductive) load)




$Q$  is negative  
current leads voltage  
 $\theta_v - \theta_i > 0$ .

leading (capacitive) load

$$S = \vec{V}_{eff} \cdot \vec{I}_{eff}^* = \frac{1}{2} \vec{V} \cdot \vec{I}^*$$

$$P = |\vec{I}_{eff}|^2 R = \frac{1}{2} I_m^2 R \quad ; \quad Q = |\vec{I}_{eff}^*|^2 X = \frac{1}{2} I_m^2 X$$

Example conti:

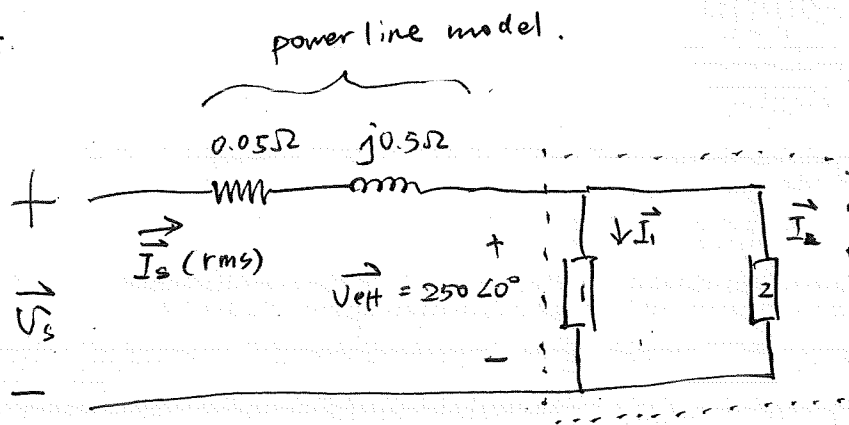

We have already calculated that: (in the previous lecture note)

The complex power consumed by the parallelly connected load, Load 1 + Load 2 is:

$$S = 20000 + j10000 \text{ VA.}$$

Now, we assume a simplified model of the power line, it has impedance of  $0.05\Omega + j0.5\Omega$ .

Find: ① The apparent power to support the loads.

② The magnitude of  $\vec{I}_s$ ,

③ The average power lost in the transmission line.

$$S = 20000 + j10000 \Rightarrow |S| = \sqrt{(20K)^2 + (10K)^2} = \boxed{22.36 \text{ KVA}} \quad \text{①}$$

$$\vec{I}_s = ? \quad S = \vec{V}_{eff} \cdot \vec{I}_{eff}^* = \vec{V}_{eff} \cdot \vec{I}_s^* = 20K + j10K$$

$$\vec{I}_s^* = \frac{20K + j10K}{250} = 80 + j40 \text{ A.}$$

$$\vec{I}_s = 80 - j40 \text{ A, } |\vec{I}_s| = \sqrt{80^2 + 40^2} = \boxed{89.44 \text{ A}} \quad \text{②}$$

$$\text{③ } P_{line} = |\vec{I}_s|^2 \cdot R = 89.44^2 \times 0.05 = \boxed{400 \text{ W}} \quad \text{③}$$

b. Remember that, all voltages and currents in this example is "rms".

# Passive power factor correction. (PFC)


We have extra power loss due to the reactive power.

We can use capacitor / inductor to cancel it!

We know that the load has:

$$S = 20k + j10k$$

$$|S| = 22.36 \text{ kVA}$$

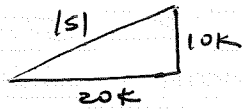

$Q > 0$ , inductive load.

if: we add sth to the parallel circuit, hopefully,

We will have:  $S_{pfc} = 20k + j10k - \underline{j10k} = 20k$ .

$$S_{pfc} = -j10k \quad Q_c = -10k = \frac{|V_{eff}|^2}{X_c} = \frac{250^2}{X_c}$$


capacitor.  $\Rightarrow X_c = \frac{250^2}{-10k} = -6.25 \Omega$

Remember,  $Z = R + jX$  for capacitor,  $R=0$ .  $X = \frac{-1}{\omega C}$

$$-\frac{1}{\omega C} = -6.25, \quad \omega = 2\pi f = 2\pi \times 60 \text{ rad/s}$$

$$\Rightarrow C = \frac{1}{2\pi \times 60 \times 6.25} = 424.4 \mu\text{F}$$

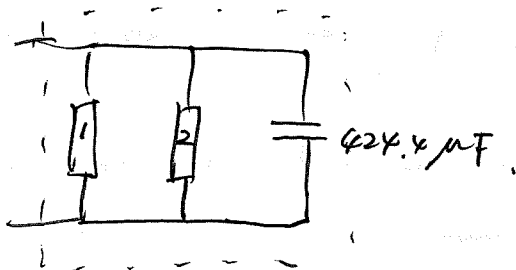With the  $424.4 \mu\text{F}$  in parallel,



The final product:

$$S = 20k, \text{ real number,}$$

$$|S| = 20k \text{ V}\cdot\text{A}, < 22.36 \text{ kVA}$$

Then let's see how much power is lost in the transmission line


$$\vec{I}_s^* = \frac{S}{V_{eff}} = \frac{20k}{250} = 80 + j0 \text{ A}; \quad \vec{I}_s = 80 \text{ A. real!}$$

$$P = |\vec{I}_s|^2 \cdot R = 80^2 \times 0.05 = 320 \text{ W}, < 400 \text{ W. we save some power!}$$

# Maximum Power Transfer.


Systems that transmit information via electric signals depends on being able to deliver the maximum of power from the source to the load.

For DC circuit:

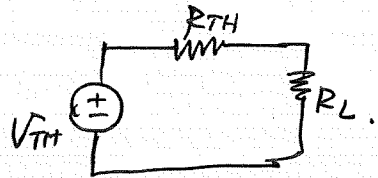

To get maximum power:  $R_L = R_{TH}$ .

For AC circuit:

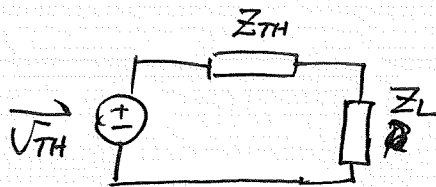

Let's see the conclusion:

To get maximum power:  $Z_{TH} = R + jX$ .

$Z_L = R - jX$ .

This is simply because:  $R_{TH} = R_L$  for the real part to extract the max power.

and for the imaginary part:

just cancel it!


or:  $Z_L = Z_{TH}^*$

easy!

So, if  $Z_{TH}$  is inductive, use capacitive load,

$Z_{TH}$  is capacitive, use inductive load.

Then let's explain why.

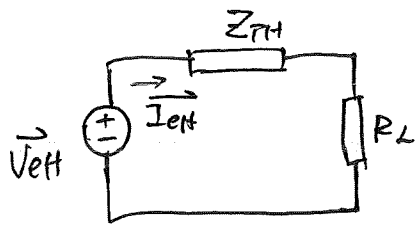

$$Z_{TH} = R_{TH} + j X_{TH}$$

$$Z_L = R_L + j X_L$$

$$\vec{I}_{eff} = \frac{\vec{V}_{eff}}{R_{TH} + j X_{TH} + R_L + j X_L}$$

Let's look at the power delivered to the  $Z_L$ :

$$P = |\vec{I}_{eff}|^2 \cdot R_L = \frac{|\vec{V}_{eff}|^2 R_L}{(R_{TH} + R_L)^2 + (X_{TH} + X_L)^2}$$

⇒ maximum?

$$\frac{\partial P}{\partial X_L} = \frac{-|\vec{V}_{eff}|^2 \cdot 2 R_L (X_L + X_{TH})}{[(R_L + R_{TH})^2 + (X_L + X_{TH})^2]^2}$$

$$\frac{\partial P}{\partial R_L} = \frac{|\vec{V}_{eff}|^2 \cdot [(R_L + R_{TH})^2 + (X_L + X_{TH})^2 - 2 R_L (R_L + R_{TH})]}{[(R_L + R_{TH})^2 + (X_L + X_{TH})^2]^2}$$


$$\frac{\partial P}{\partial X_L} = 0, \quad X_L = -X_{TH}. \quad \checkmark$$

$$\frac{\partial P}{\partial R_L} = 0, \quad (R_L + R_{TH})^2 = 2 R_L (R_L + R_{TH})$$

$$\Rightarrow R_L + R_{TH} = 2 R_L \Rightarrow R_{TH} = R_L$$

$$\Rightarrow X_L = -X_{TH}, \quad R_L = R_{TH}$$

$$Z_L = Z_{TH}^*$$

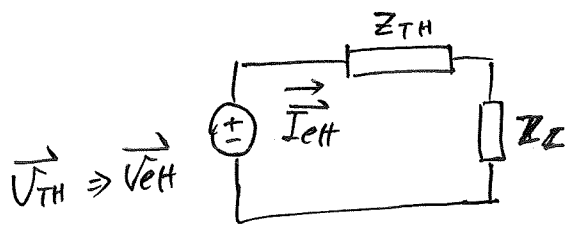

Given  $Z_L = Z_{TH}^*$ , what is the maximum power transferred to the load?

$$\vec{I}_{eff} = \frac{\vec{V}_{eff}}{Z_{TH} + Z_L} = \frac{\vec{V}_{eff}}{2R_L}$$


$$P = |\vec{I}_{eff}|^2 \cdot R_L = \frac{|\vec{V}_{eff}|^2}{4R_L^2} \times R_L = \frac{|\vec{V}_{eff}|^2}{4R_L}$$

If,  $V$  &  $I$  are in Amplitude form.

remember:  $|\vec{V}_{eff}| = \frac{V_m}{\sqrt{2}}$ ,  $|\vec{I}_{eff}| = \frac{I_m}{\sqrt{2}}$

$$P = \frac{|\vec{V}|^2}{8R_L} = \frac{V_m^2}{8R_L}$$

Example:

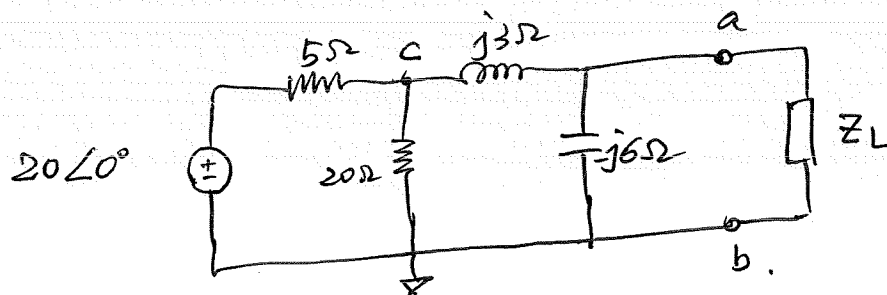

find  $Z_L$  for maximum power transfer.

① find  $V_{TH}$  &  $Z_{TH}$ .

$$\frac{\vec{V}_c - 20}{5} + \frac{\vec{V}_c}{20} + \frac{\vec{V}_c}{-j3} = 0 \Rightarrow \vec{V}_c = 5.76 - j7.68$$

$$\vec{V}_{ab} = \vec{V}_{TH} = \vec{V}_c \times \frac{-j6}{-j6 + j3} = \vec{V}_c \times 2 = 11.52 - j15.36 = 19.2 \angle -53.13^\circ \text{ V}$$


(if just to find  $Z_L$ , we don't need to find  $\vec{V}_{TH}$ , though)

$$Z_{TH} \Rightarrow [5 \parallel 20 + j3] \parallel (-j6)$$

$$\Rightarrow \frac{(4 + j3) \times (-j6)}{4 + j3 - j6} = 5.76 - j1.68 \Omega$$

$$Z_L = Z_{TH}^* = 5.76 + j1.68 \Omega$$

Then:

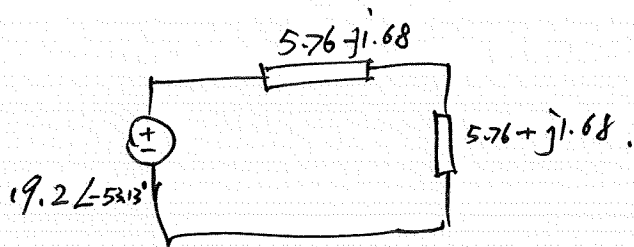

How much <sup>average</sup> power is delivered?

$$\vec{V}_{TH} = 19.2 \angle -53.13^\circ, \quad |\vec{V}_{eff}| = \frac{19.2}{\sqrt{2}} = 13.58 \text{ V}$$

$$P_{max} = \frac{|\vec{V}_{eff}|^2}{4R_L} = \frac{13.58^2}{4 \times 5.76} = 8 \text{ W}$$