
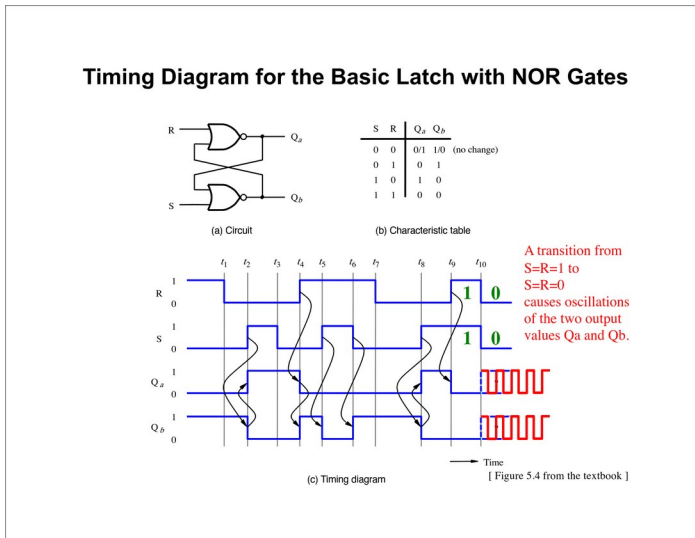


Latches


Basic NOR Latch:

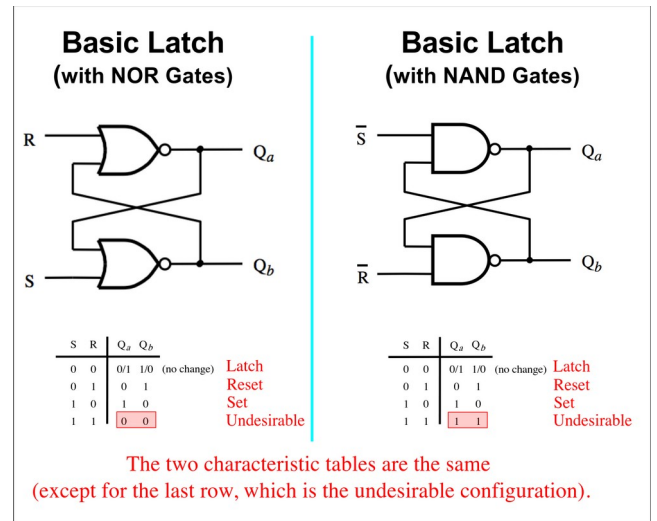

Basic NAND Latch:




Gated SR Latches:

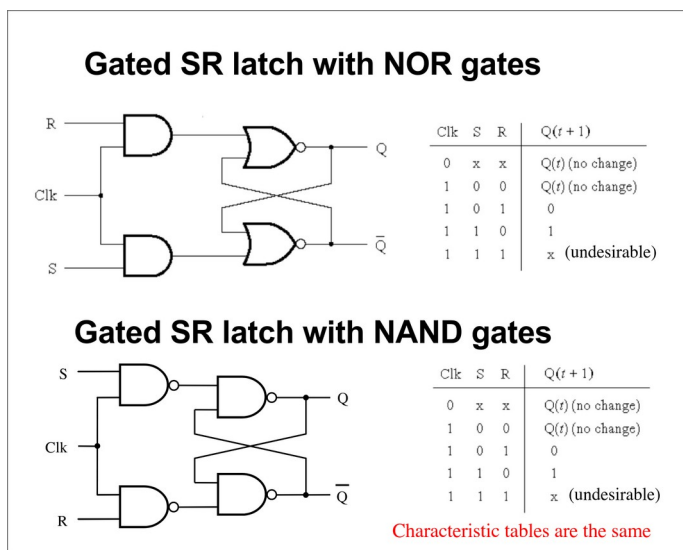


*A transition from S=R=1 to S=R=0 causes the output of the SR latch to oscillate between 0 and 1, until random factors (gate delays & wire lengths) cause it to settle on an unpredictable value

Gated D Latch with NAND/XOR Gates:

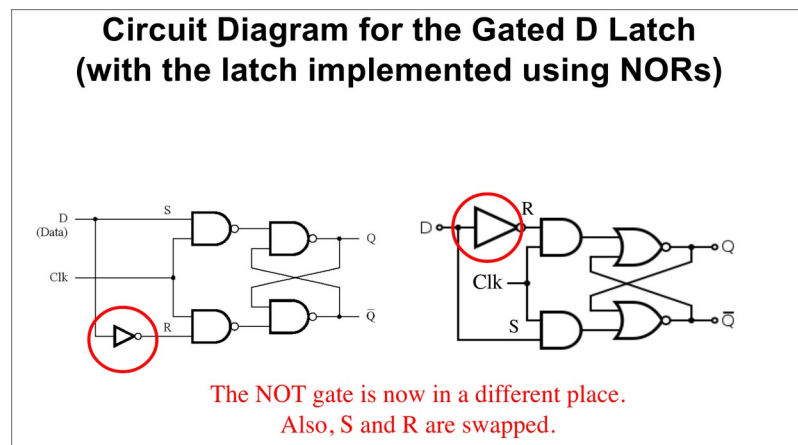


Setup and hold times

 


Setup time (t_{su}) – the minimum time that the D signal must be stable prior to the negative edge of the Clock signal.

Hold time (t_h) – the minimum time that the D signal must remain stable after the negative edge of the Clock signal.


Master-Slave D Flip-Flop:

 


Pos/Neg Edge-Triggered D Flip-Flops:

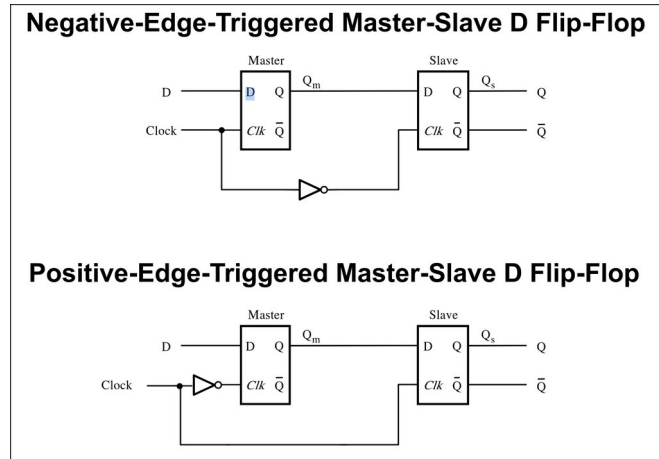

 
Positive-Edge-Triggered D Flip-Flop with Asynchronous Clear and Preset



 
Complete Wiring Diagram for a Positive-Edge-Triggered D Flip-Flop:




T Flip-Flop w/ D Flip-Flop:

 


JK Flip-Flop w/ D Flip-Flop:

 


D Flip-Flop w/ T Flip-Flop:

 


JK Flip-Flop w/ T Flip-Flop

 

T Flip-Flop w/ JK Flip-Flop:

 


D Flip-Flop w/ JK Flip-Flop:

 


Registers


1-bit Parallel Access Register

 


2-bit Parallel Access Register

 

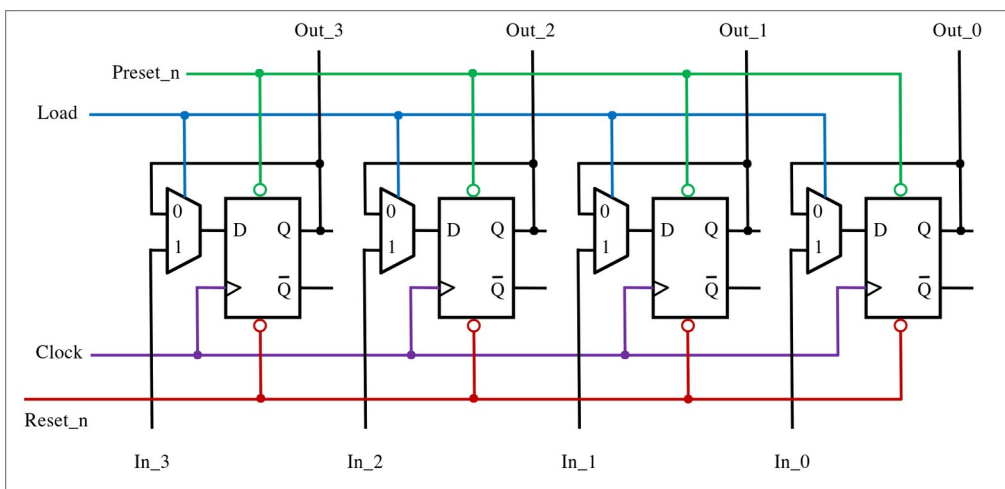4-bit Parallel Access Register w/ Async Preset/Clear



 Parallel-access shift left/right register




$C\{1,0\} = 00$: do nothing

$C\{1,0\} = 01$: shift left

$C\{1,0\} = 10$: shift right


$C\{1,0\} = 11$: load from input

Register File:

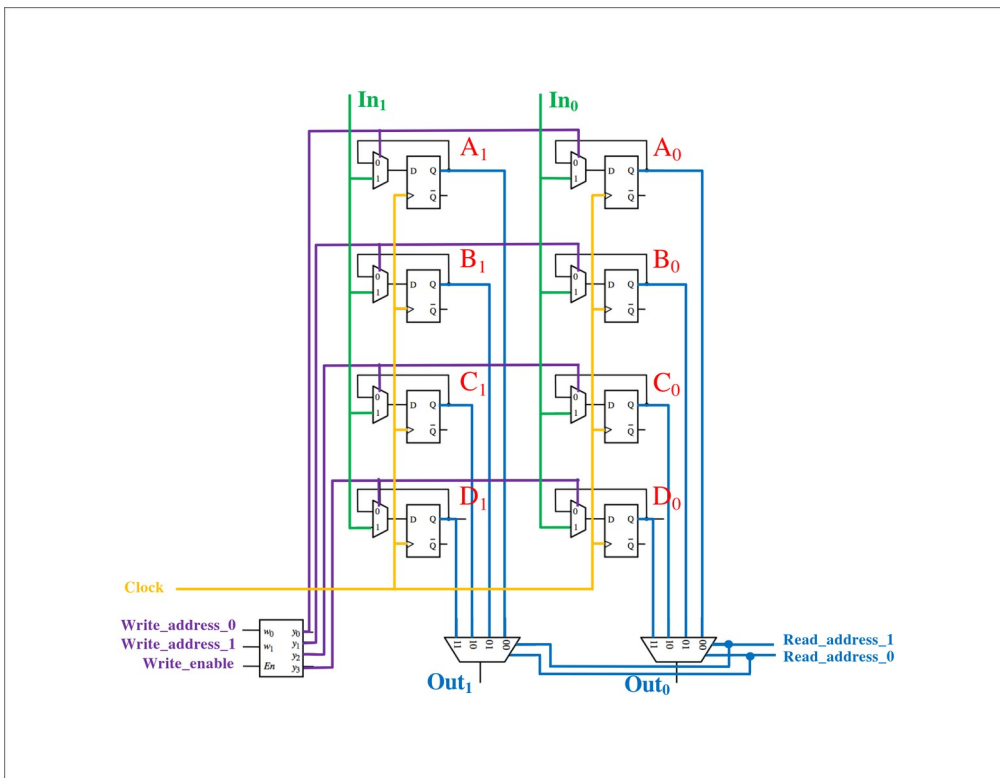

Counters

3-bit Down Counter

 


The first flip-flop changes on the positive edge of the clock

The second flip-flop changes on the positive edge of Q_0

The third flip-flop changes on the positive edge of Q_1

3-bit Up Counter

 


The first flip-flop changes on the positive edge of the clock


The second flip-flop changes on the positive edge of \bar{Q}_0

The third flip-flop changes on the positive edge of \bar{Q}_1


4-bit Synchronous Up Counter

 

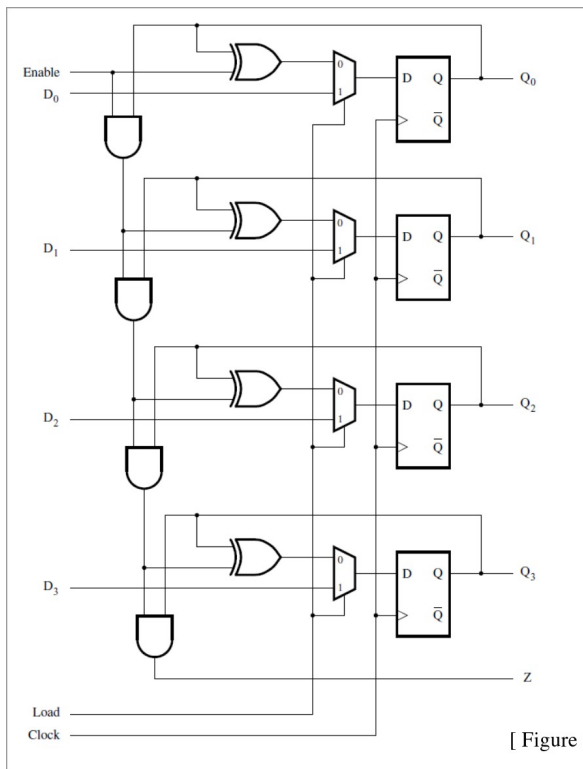
Synchronous 4-bit Up Counter w/ Parallel Load using D Flip-Flops



Mod-6 Up Counter w/ Synchronous Reset

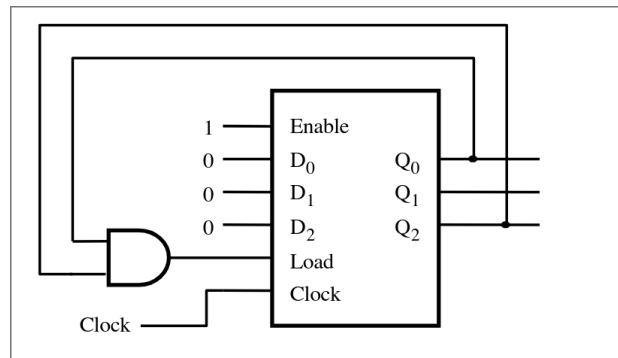


Mod-6 Up Counter w/ Async Reset

 

*For a counter that doesn't count to a power of 2, a sync/async reset on all flip-flops should occur when the max value is reached (e.g. above we reset on $Q_2 * Q_0 = 101 = 6$)


Finite State Machines

Moore Implementation

 


*The output depends only on the current state

Mealy Machine

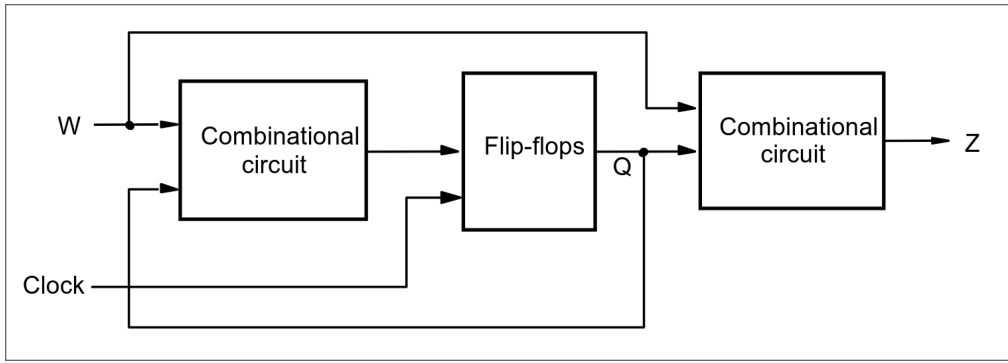


*The output depends on the current state **and** the current inputs

Serial Adder

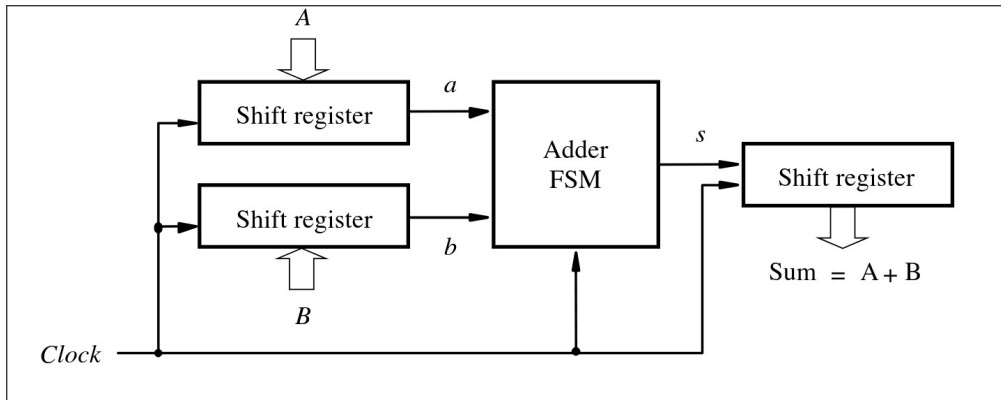


Mealy Implementation of FSM

Moore Machine Implementation of FSM

 

Present state	Next state				Output s
	ab=00	01	10	11	
G ₀	G ₀	G ₁	G ₁	H ₀	0
G ₁	G ₀	G ₁	G ₁	H ₀	1
H ₀	G ₁	H ₀	H ₀	H ₁	0
H ₁	G ₁	H ₀	H ₀	H ₁	1



State table for the serial adder FSM

 

Present state	Next state				Output s			
	ab=00	01	10	11	00	01	10	11
G	G	G	G	H	0	1	1	0
H	G	H	H	H	1	0	0	1

Mealy FSM Circuit Diagram

Moore FSM Circuit Diagram

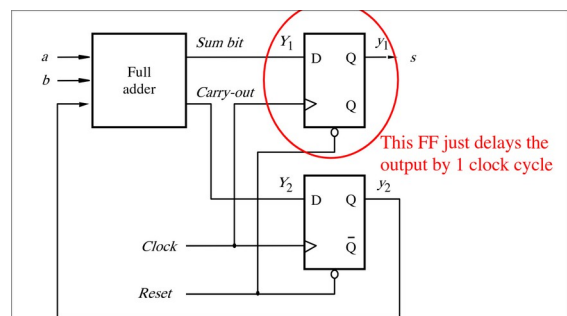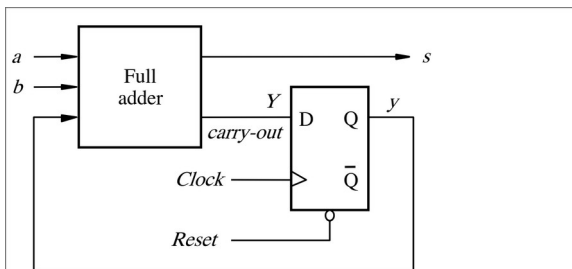


$s = \text{XOR}(\text{XOR}(a, b), y)$ (sum bit from FA)
 $Y = ab + ay + by$ (carry bit from FA)

$Y_1 = a \oplus b \oplus y_2$ (sum bit from FA)
 $Y_2 = ab + ay_2 + by_2$ (carry bit from FA)
 $s = y_1$

Arbiter FSM Diagram

Arbiter State Table

Arbiter State-Assigned Table

 


	r ₁ r ₂ =00	01	10	11	Output
A	A C	B B	B B	00	
B	A A	B B	B B	10	
C	A C	A C	A C	01	


Present state	Next state				Output
	r ₁ r ₂ =00	01	10	11	
A	00	00	10	01	00
B	01	00	00	01	10
C	10	00	10	00	01
	11	dd	dd	dd	dd

Arbiter Output Expressions

 Output expressions
 $g_1 = Y_1$
 $g_2 = Y_2$



Arbiter Circuit Diagram

 

State Minimization:

- 1. Group all states by their outputs
- 2. Ensure that all for all k (every set of inputs), for each group G, each state in G has the same k-successor (next state for input k). If not, then partition G by the next-state that k-leads to.
- 3. Repeat (2.) until no more partitions are made

SSC Circuit Analysis:

- 1. Find the logic expressions for all next state variables and all outputs.
- 2. Derive the state-assigned table from these logic expressions
- 3. Derive the state table from the state-assigned table
- 4. Derive the state diagram from the state table

Register Machine Instructions

- INC reg, next_step
- DEB reg, next_step, branch_to_if_zero
- END

Example Register Machine Program

STEP	INSTRUCTION	REGISTER	GO TO STEP	[BRANCH TO STEP]
1.	Deb	1	2	3
2.	Inc	2	1	
3.	End			